

Total No. of printed pages = 3

END SEMESTER EXAMINATION – 2022

Semester : 4th

Subject Code : Co-406

DIGITAL ELECTRONICS

Full Marks – 35

Time – 1½ hours

The figures in the margin indicate full marks for the questions.

Instructions :

1. All questions of PART – A are compulsory.
2. Answer any two from Q. Nos. 2 to 4 and Q. No. 5 is compulsory of PART – B.

PART – A

Marks – 12

1. Fill in the blanks : 1×12=12

(a) An Inverter is also known as NOT gate.

(b) NAND and NOR gates are also known as universal gates.

[Turn over

- (c) Logic gate operates on the principle of Boolean algebra.
- (d) The basic storage element in a digital system is flip flop.
- (e) A counter can be described as a pulse machine.
- (f) Flip-flop is a sequential logic circuit.
- (g) A ring counter has 2 flip-flops.
- (h) What Arithmetic circuit is used to subtract? Binary
- (i) Rom are used to store data that generally can not be easily changed.
- (j) CD-ROM stands for Compact Disc Read only memory.
- (k) Registers and Counters are designed using flip flop.
- (l) Multiplexer is represented by mux.

PART - B

Marks - 23

2. (a) Prove the following using Truth table: 2
 $A + A'B = A + B$.
- (b) Draw the logic diagram for the Boolean expression $Y = AC + A'B$ using basic gates. 2

12/Co-406/DE/4th Sem (2)

(c) Draw OR and AND gate using NAND gate only. $2+2=4$

3. Classify digital ICs. Write their characteristic features. 8

4. (a) What are the differences between Combinational logic circuit and Sequential logic circuit. 4

(b) What is Karnaugh map ? Define Pair, Quad and Octet. $1+3=4$

5. Write short notes on any two : $3\frac{1}{2} \times 2 = 7$

(a) Half adder

(b) Applications of LCD and LED displays

(c) Semiconductor memory

(d) TTL Circuit

(e) Seven segment display.