

Total No. of printed pages = 6

El-401/ECN/4th Sem/2018/M

ELECTRICAL CIRCUIT AND NETWORK

Full Marks – 70

Time – Three hours

The figures in the margin indicate full marks
for the questions.

PART – A

Marks – 25

Time – One hour

Answer *all* the questions.

1. Fill in the blanks : 1×10=10

(a) Norton's theorem can be applied only in _____
circuit.

(b) A network having one or more than one source
of e.m.f is known as _____ network.

(c) In a parallel RLC circuit, with $X_L > X_C$ the
circuit behaves as _____.

[Turn over

(d) Admittance is equal to the reciprocals of _____.

(e) Number of cycles per second is called _____.

(f) The equation of true power is _____.

(g) The ratio of true power by apparent power is called _____.

(h) Negative phase angle means _____.

(i) In delta connected three phase system, the line voltage = _____.

(j) In the two parallel branches of a parallel circuit, more current will flow through that branch which has _____ impedance.

2. State true or false :

$$1 \times 10 = 10$$

(a) Kirchhoff's first law is based on the principle of law of conservation of charge.

(b) The total resistance in a series circuit is always less than the least resistor.

(c) The voltages across all components in a parallel circuit are equal.

- (d) Thevenin's resistance is found by removing voltage sources along with their internal resistance.
- (e) An ideal voltage source should have zero source resistance.
- (f) The superposition theorem requires as many circuits to be solved as there are sources.
- (g) The time period of a wave is same as frequency.
- (h) Form factor is the ratio of r.m.s value and average value.
- (i) At series resonance, applied voltage V = voltage across R .
- (j) The power factor of pure capacitive circuit is 1.

3. Multiple choice questions : 1×5=5

- (a) In a star-connected system, the current flowing through the line is :
 - (i) Greater than the phase current
 - (ii) Equal to the phase current
 - (iii) Lesser than the phase current
 - (iv) None of these.

(b) Ohmic value of capacitive coil is called :

- (i) Impedance
- (ii) Resistance
- (iii) Capacitive reactance
- (iv) Inductive reactance

(c) In a three phase AC circuit, the sum of all three generated voltage is :

- (i) Infinite
- (ii) One
- (iii) Zero
- (iv) None of the above.

(d) In case of inductive circuit, frequency is _____ proportional to the inductive reactance.

- (i) directly
- (ii) inversely
- (iii) No effect

(e) Unit of admittance is :

- (i) Ohm
- (ii) Siemens
- (iii) Henry
- (iv) Farad.


PART – B

Marks – 45

Time – Two hours

Answer any *three* questions.

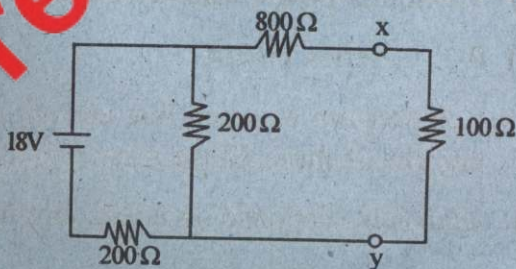4. (a) Define parameters, non-linear circuit, bilateral circuit and active network. 6
- (b) A circuit consisting of three resistances of 12Ω , 18Ω and 36Ω respectively joined in parallel is connected in series with a fourth resistance R . The whole circuit is supplied at $60V$ and it is found the power dissipated in 12Ω resistance is 36 W . Determine the value of " R " and power absorbed in the parallel group. 9
5. (a) Prove the reciprocity theorem. 5
- (b) Find the voltage across 10 ohm resistor by constructing Norton's equivalent circuit in the figure to the left of terminals x-y. 10



6. (a) A coil of resistance 12Ω and inductive reactance of 25Ω is connected in series with a capacitive reactance of 15Ω . The combination is connected to a supply of 230V, 50 Hz. Find 9

(i) Circuit impedance

(ii) Current

(iii) Power consumed.

- (b) Define RMS value, average value and form factor. 6

7. In a series parallel circuit the parallel branches A and B are in series with C. The impedances are $Z_A = 5 + j3$, $Z_B = 9 - j7$ and $Z_C = 6 + j5$. If the voltage applied to the circuit is 180V at 50 Hz. calculate : 15

(a) Current I_A , I_B and I_C .

(b) The total power factor for the whole circuit.

8. Write short notes on any three : $5 \times 3 = 15$

(a) Maximum power transfer theorem

(b) R-L-C series circuit

(c) Relationship between line current and phase current of three phase star-connect system.

(d) Transient response on a R-L circuit.